

EE241: COMPUTER TOOLS FOR ELECTRICAL ENGINEERS
PROJECT-2

Due: December 25, 2017

Instructor: Arda D. Yalçinkaya

Total: 25points.

As a design engineer of a small electronics company, you are given your first task. After evaluating the design choices, you finally decide to implement a wheat-stone bridge circuit (which is shown in Figure 1) for the readout electronics of the company's new force sensor.

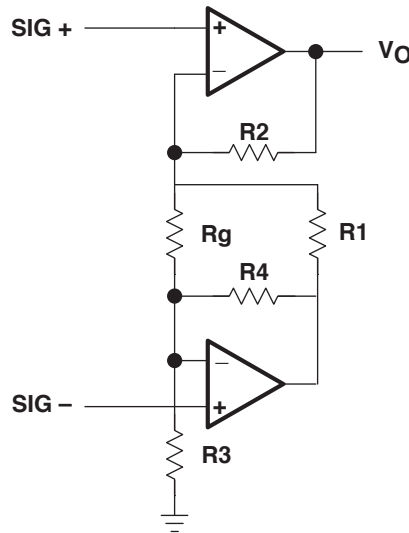


Figure 1 - $R_1=R_2=2k$, $R_3=R_4=1k$, $R_g=1k$

a. (7p) Implement the circuit in PSPICE containing OPAMPS shown below (Figure 2). Determine the output voltage when $V_{in} = ((SIG +) - (SIG -))$ varies between -5V and 5V.

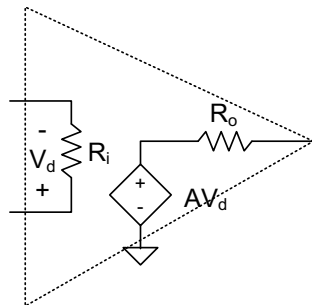


Figure 2- $R_i=150k\Omega$, $R_o=250\Omega$, $A=5500$

b. Implement the circuit in PSPICE containing TL072 OPAMPS from Texas Instruments (<http://focus.ti.com/docs/prod/folders/print/tl072.html>). You should bias the OPAMPS with +/- 10V.

i. (7p) Determine the output voltage when $V_{in} = ((SIG +) - (SIG -))$ varies between -5V and 5V. Compare your results with part (a).

ii. (6p) Assume $V_{in}=1.2V$. Simulate the circuit behavior to obtain the range of V_{out} when you use 25% tolerance resistors.

iii. (5p) Determine the output voltage when V_{in} is a 1.5V peak-to-peak sine wave at 1 kHz.

NOTES:

- Please return a short report answering the questions above. You should include in your report all the schematics, probe screens, custom libraries that you used, etc.
- This is an individual project. Please type and sign the following statement:
"I pledge my honor that I have neither given nor received any unauthorized aid on this assignment."

Signature: